
Q

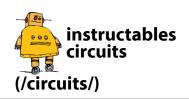

Projects (/circuits/projects/)

Community (/circuits/community/)

Let's Make...

# **Control DC and Stepper Motors With L298N Dual Motor Controller Modules and Arduino**

By tronixlabs (/member/tronixlabs/) in Circuits (/circuits/) > Arduino (/circuits/arduino/projects/)


492,811

341

66

Download

**Favorite** 

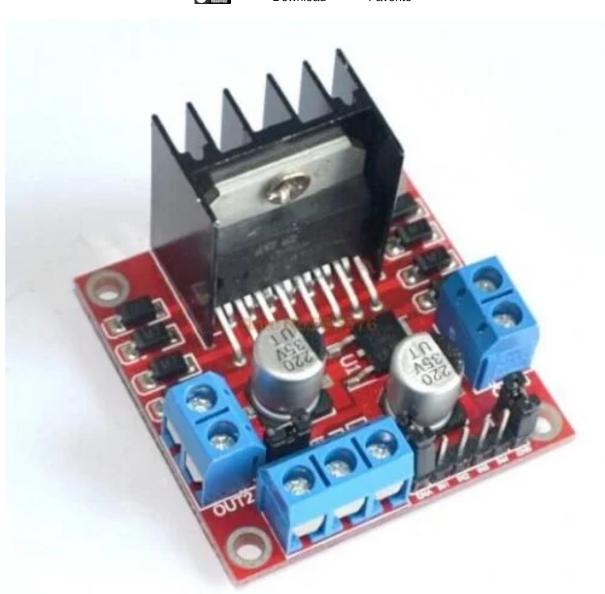

(/member/tronixlabs/)



hobbyist electronics from adafruit, DFRobot, Freetronics, Seeed Studio and more! More About tronixlabs » (/member/tronixlabs/)

You don't have to spend a lot of money to control motors with an Arduino or compatible board. After some hunting around we <u>found a neat motor control module based (http://troni xlabs.com/robotics/motor-controllers/I298n-dual-motor-controller-module-2a/)</u> on the L298N H-bridge IC that can allows you to control the speed and direction of two DC motors, or control one bipolar stepper motor with ease.

The <u>L298N H-bridge module (http://tronixlabs.com/robotics/motor-controllers/I298n-dual-motor-controller-module-2a/)</u> can be used with motors that have a voltage of between 5 and 35V DC. With the module used in this tutorial, there is also an onboard 5V regulator, so if your supply voltage is up to 12V you can also source 5V from the board.

So let's get started!




## **Teacher Notes**

Teachers! Did you use this instructable in your classroom?

Add a Teacher Note to share how you incorporated it into your lesson.

Add Teacher Note

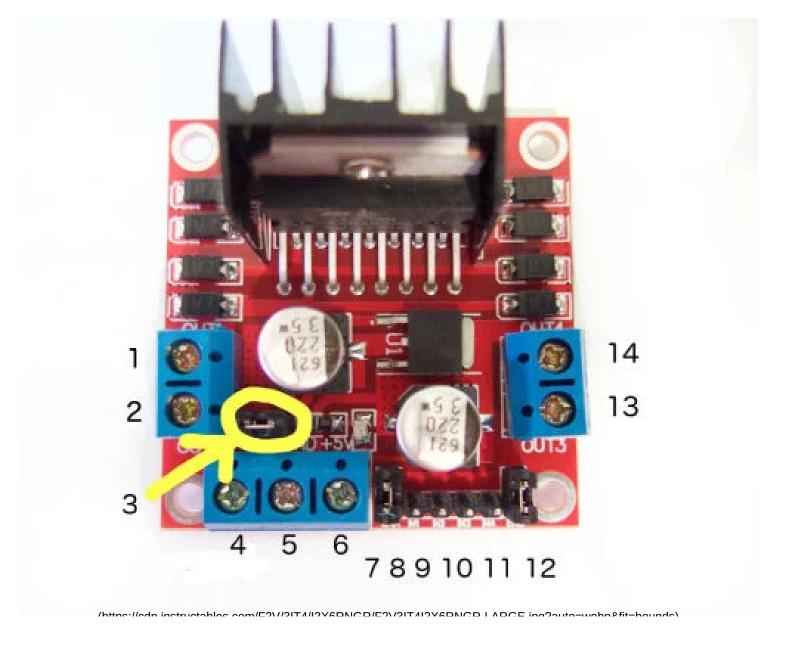**Step 1: Understanding the L298 Module Connections** 



First we'll run through the connections, then explain how to control DC motors then a stepper motor. At this point, review the connections on the <u>L298N H-bridge module (http://</u>

tronixlabs.com/robotics/motor-controllers/I298n-dual-motor-controller-module-2a/).

Consider the image – match the numbers against the list below the image:

- 1. DC motor 1 "+" or stepper motor A+
- 2. DC motor 1 "-" or stepper motor A-
- 3. 12V jumper remove this if using a supply voltage greater than 12V DC. This enables power to the onboard 5V regulator
- 4. Connect your motor supply voltage here, maximum of 35V DC. Remove 12V jumper if >12V DC


5. GND 6. 5V output if 12V jumper in place, ideal for powering your Arduino (etc) 7. DC motor 1 enable jumper. Leave this in place when using a stepper motor. Connect to PWM output for DC motor speed control. 8. IN1 9. IN2 10. IN3 11. IN4 12. DC motor 2 enable jumper. Leave this in place when using a stepper motor. Connect to PWM output for DC motor speed control 13. DC motor 2 "+" or stepper motor B+ 14. DC motor 2 "-" or stepper motor B-

**Step 2: Controlling DC Motors** 

Comment

Download

? Ask Question

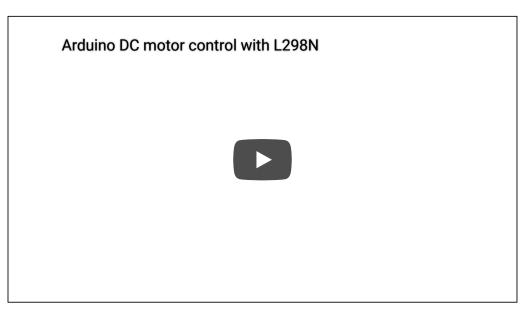

- Add Tip



To control one or two DC motors is quite easy with the <u>L298N H-bridge module (http://troni</u>xlabs.com/robotics/motor-controllers/1298n-dual-motor-controller-module-2a/). First connect each motor to the A and B connections on the L298N module.

If you're using two motors for a robot (etc) ensure that the polarity of the motors is the same on both inputs. Otherwise you may need to swap them over when you set both motors to forward and one goes backwards!

Next, connect your power supply – the positive to pin 4 on the module and negative/GND to pin 5. If you supply is up to 12V you can leave in the 12V jumper (point 3 in the image above) and 5V will be available from pin 6 on the module.

This can be fed to your Arduino's 5V pin to power it from the motors' power supply. Don't forget to connect Arduino GND to pin 5 on the module as well to complete the circuit. Now you will need six digital output pins on your Arduino, two of which need to be PWM (pulsewidth modulation) pins.

PWM pins are denoted by the tilde (" $\sim$ ") next to the pin number, for example in the image of the Arduino Uno's digital pins.

Finally, connect the Arduino digital output pins to the driver module. In our example we have two DC motors, so digital pins D9, D8, D7 and D6 will be connected to pins IN1, IN2, IN3 and IN4 respectively. Then connect D10 to module pin 7 (remove the jumper first) and D5 to module pin 12 (again, remove the jumper).

The motor direction is controlled by sending a HIGH or LOW signal to the drive for each motor (or channel). For example for motor one, a HIGH to IN1 and a LOW to IN2 will cause it to turn in one direction, and a LOW and HIGH will cause it to turn in the other direction.

However the motors will not turn until a HIGH is set to the enable pin (7 for motor one, 12 for motor two). And they can be turned off with a LOW to the same pin(s). However if you need to control the speed of the motors, the PWM signal from the digital pin connected to the enable pin can take care of it.

This is what we've done with the DC motor demonstration sketch. Two DC motors and an Arduino Uno are connected as described above, along with an external power supply. Then enter and upload the following sketch:

```
// connect motor controller pins to Arduino digital pins
// motor one
int enA = 10;
int in1 = 9;
int in2 = 8;
// motor two
int enB = 5;
int in3 = 7;
int in4 = 6;
void setup()
  \ensuremath{//} set all the motor control pins to outputs
  pinMode(enA, OUTPUT);
  pinMode(enB, OUTPUT);
  pinMode(in1, OUTPUT);
  pinMode(in2, OUTPUT);
  pinMode(in3, OUTPUT);
  pinMode(in4, OUTPUT);
}
void demoOne()
  // this function will run the motors in both directions at a fixed speed
  // turn on motor A
  digitalWrite(in1, HIGH);
  digitalWrite(in2, LOW);
  // cot chood to 200 out of necesible range 0-255
```


So what's happening in that sketch? In the function demoOne() we turn the motors on and run them at a PWM value of 200. This is not a speed value, instead power is applied for 200/255 of an amount of time at once.

Then after a moment the motors operate in the reverse direction (see how we changed the HIGHs and LOWs in the digital Write () functions?). To get an idea of the range of speed possible of your hardware, we run through the entire PWM range in the function demoTwo() which turns the motors on and them runs through PWM values zero to 255 and back to zero with the two for loops.

Finally this is demonstrated in the video on this page – using our well-worn tank chassis with two DC motors.



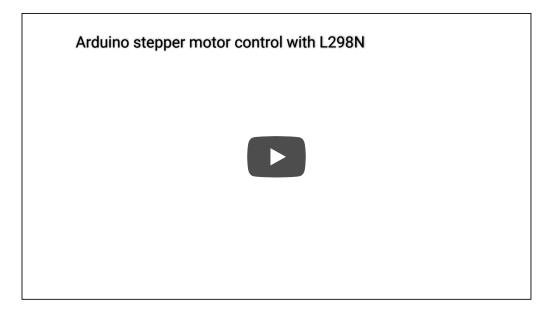Step 3: Controlling a Stepper Motor With Arduino and L298N





Stepper motors may appear to be complex, but nothing could be further than the truth. In this example we control a typical NEMA-17 stepper motor that has four wires, as shown in the image on this step.

It has 200 steps per revolution, and can operate at at 60 RPM. If you don't already have the step and speed value for your motor, find out now and you will need it for the sketch.

The key to successful stepper motor control is identifying the wires – that is which one is which. You will need to determine the A+, A-, B+ and B- wires. With our example motor these are red, green, yellow and blue. Now let's get the wiring done.

Connect the A+, A-, B+ and B- wires from the stepper motor to the module connections 1, 2, 13 and 14 respectively. Place the jumpers included with the L298N module over the pairs at module points 7 and 12. Then connect the power supply as required to points 4 (positive) and 5 (negative/GND).

Once again if your stepper motor's power supply is less than 12V, fit the jumper to the module at point 3 which gives you a neat 5V power supply for your Arduino. Next, connect L298N module pins IN1, IN2, IN3 and IN4 to Arduino digital pins D8, D9, D10 and D11 respectively.

Finally, connect Arduino GND to point 5 on the module, and Arduino 5V to point 6 if sourcing 5V from the module. Controlling the stepper motor from your sketches is very simple, thanks to the Stepper Arduino library included with the Arduino IDE as standard.

To demonstrate your motor, simply load the stepper\_oneRevolution sketch that is included with the Stepper library. To find this, click the File > Examples > Stepper menu in the Arduino IDE.

Finally, check the value for

```
const int stepsPerRevolution = 200;
```

in the sketch and change the 200 to the number of steps per revolution for your stepper motor, and also the speed which is preset to 60 RPM in the following line:

```
myStepper.setSpeed(60);
```

Now you can save and upload the sketch, which will send your stepper motor around one revolution, then back again. This is achieved with the function

```
myStepper.step(stepsPerRevolution); // for clockwise  myStepper.step(-stepsPerRevolution); // for anti-clockwise
```

Finally, a quick demonstration of our test hardware is shown in the video on this step.

So there you have it, an easy an <u>inexpensive way to control motors with your Arduino or compatible board (http://tronixlabs.com/robotics/motor-controllers/1298n-dual-motor-controller-module-2a/)</u>. And if you enjoyed this article, or want to introduce someone else to the interesting world of Arduino – check out my book (now in a fourth printing!) "<u>Arduino Work shop (http://tronixlabs.com/arduino/arduino-workshop-a-hands-on-introduction-with-65-p rojects-by-john-boxall/)</u>".



## **5 People Made This Project!**




## See 1 More

Did you make this project? Share it with us!


I Made It!


## **Recommendations**

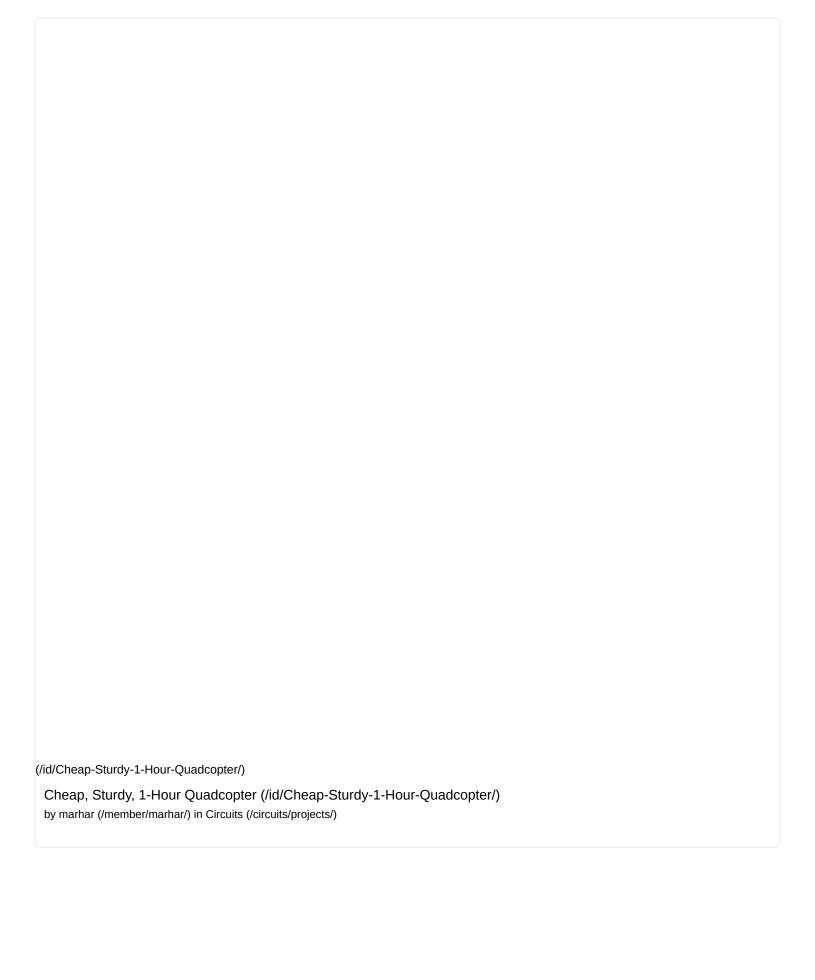






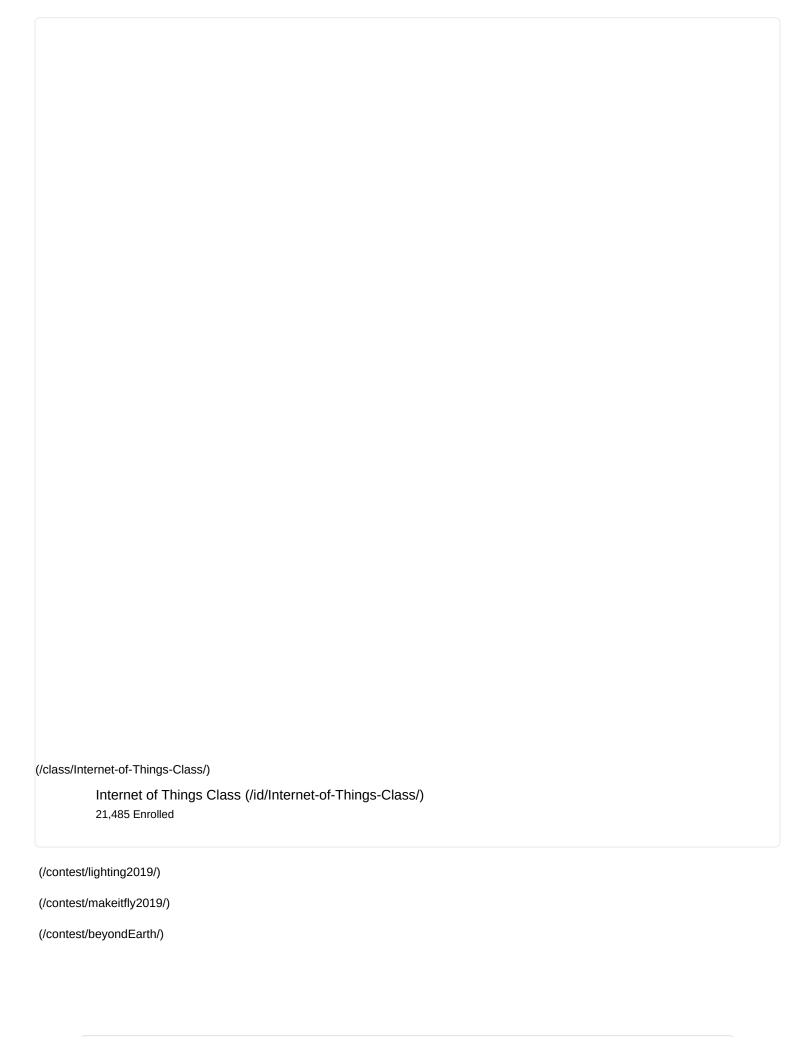

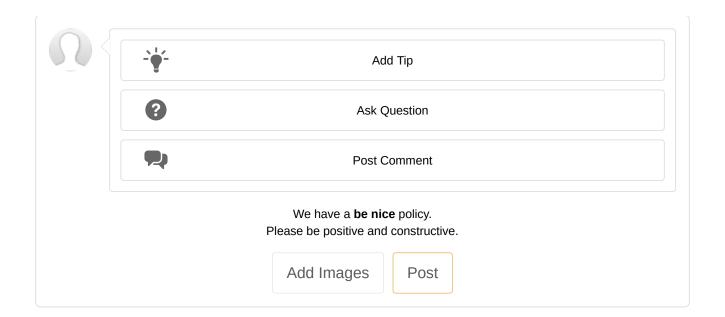

## 66 Discussions

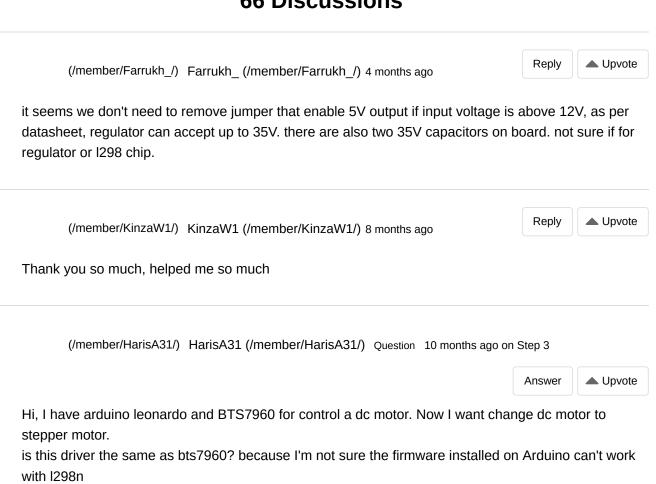

(/member/SEB23232323/) SEB23232323 (/member/SEB23232323/) 12 months ago

 I am controlling a 12 V DC motor, the input voltage (between pin 4 and 5) is 11,68 V, I am using a pwm value of 255 and when I measure the output voltage to the motor (between pin 14 and 13) I found 6.28 V. Is that normal, because it is suppose to be equal to the input voltage (11.68V). (only one motor is connected)

```
Reply
                                                                                            Upvote
       (/member/vertex28/) vertex28 (/member/vertex28/) 2 years ago
Hello
great job. In step 1, state 3
"12V jumper - remove this if using a supply voltage greater than 12V DC. This enables power to the
onboard 5V regulator"
I use 14.4 V baterry. when i remove jumper, "L298 module" shut down, if i put jumper back i get only
around 5v to DC motor. I control motor through bluetooth modul. How to get 12V from "L298 module".
THANKS A LOT
This is code i used
int LED=13;
volatile int state = LOW;
char getstr;
int in1=9;
int in2=8;
int in3=7;
int in4=6;
int ENA=10;
int ENB=5;
//int ABS=135;
void _mForward()
{
//analogWrite (ENA, 200); //DOLOČIŠ HTROST MOTORJA
digitalWrite(ENA,HIGH);
digitalWrite(ENB,HIGH);
///digitalWrite(in1,LOW);
///digitalWrite(in2,HIGH);
//digitalWrite(in3,LOW);
//digitalWrite(in4,HIGH);
Serial.println("go forward!");
digitalWrite(in1, HIGH);
digitalWrite(in2, LOW);
// set speed to 200 out of possible range 0~255
}
void mBack()
{
//analogWrite (ENA, 200); //DOLOČIŠ HTROST MOTORJA
digitalWrite(ENA,HIGH);
digitalWrite(ENB,HIGH);
```

///digitalWrite(in1,HIGH);

```
///digitalWrite(in2,LOW);
//digitalWrite(in3,HIGH);
//digitalWrite(in4,LOW);
Serial.println("go back!");
digitalWrite(in1, LOW);
digitalWrite(in2, HIGH);
}
void _mleft()
//analogWrite (ENB, 200); //DOLOČIŠ HTROST MOTORJA
digitalWrite(ENA,HIGH);
digitalWrite(ENB,HIGH);
//digitalWrite(in1,LOW);
//digitalWrite(in2,HIGH);
digitalWrite(in3,HIGH);
digitalWrite(in4,LOW);
Serial.println("go left!");
}
void _mright()
//analogWrite (ENA, 200); //DOLOČIŠ HTROST MOTORJA
digitalWrite(ENA,HIGH);
digitalWrite(ENB,HIGH);
//digitalWrite(in1,HIGH);
//digitalWrite(in2,LOW);
digitalWrite(in3,LOW);
digitalWrite(in4,HIGH);
Serial.println("go right!");
}
void _mStop()
{
digitalWrite(ENA,LOW);
digitalWrite(ENB,LOW);
digitalWrite(in1,LOW); //jaz dodal - drugače tevrstice ni
digitalWrite(in2,LOW); //jaz dodal - drugače tevrstice ni
digitalWrite(in3,LOW); //jaz dodal - drugače tevrstice ni
digitalWrite(in4,LOW); //jaz dodal - drugače tevrstice ni
Serial.println("Stop!");
}
void stateChange()
{
state = !state;
digitalWrite(LED, state);
void setup()
{
pinMode(LED, OUTPUT);
Serial.begin(9600);
pinMode(in1,OUTPUT);
```

```
pinMode(in2,OUTPUT);
pinMode(in3,OUTPUT);
pinMode(in4,OUTPUT);
pinMode(ENA,OUTPUT);
pinMode(ENB,OUTPUT);
_mStop();
}
void loop()
getstr=Serial.read();
if(getstr=='F')
_mForward();
delay(10);
else if(getstr=='B')
_mBack();
delay(10);
else if(getstr=='L')
{
_mleft();
delay(10);
}
else if(getstr=='R')
_mright();
delay(10);
else if(getstr=='A')
stateChange();
else //if(getstr=='B')
{
_mStop();
}
2 replies 🗸
```

(/member/MohammadH144/) MohammadH144 (/member/MohammadH144/)

Question 1 year ago on Step 2

Answer

Upvote

Reply Upvote (/member/luhocruz/) luhocruz (/member/luhocruz/) 1 year ago Hi, my motor are working right, but he is heating so much! Up to 70°C+-. Im using a Nema 16 ZEPHYR - 9BYG218 / 2S39Q-02034S 1,2kgf 1A. My source is a 12V 10A, im using the I298n and mystepper library arduino. Can you help me? Ps: there are no charge. 1 reply ~ (/member/MaharshiP4/) MaharshiP4 (/member/MaharshiP4/) Question 1 year ago on Introduction Upvote Answer hey there, i need to connect four 12v dc motor to motor driver L298N. how can i connect it, or i have two two motor driver for that. pl..answer with proper steps how to connect. thanks in advance. Upvote Reply (/member/JeffH95/) JeffH95 (/member/JeffH95/) 1 year ago I've got something profoundly weird going on; I've double-checked my wiring and everything seems fine, but the No.1 engine does nothing. I hooked up my cheap oscilloscope to the outputs expecting to see nothing, but the signals appeared to be identical in voltage and behavior to the No.2 side. I hooked up the No.1 side to a resistor and an LED and indeed the light goes on, dims, etc. just as I would expect. I swap the motors and the motor on the No.1 side does nothing and the No. 2 side works. I'm stumped. Anyone got any suggestions? Reply Upvote (/member/mankinggeo/) mankinggeo (/member/mankinggeo/) 2 years ago Hello! Can I use L298N to control a VCR Capstan Motor (without driver)? How can I do this?

(/member/MehdiC7/) MehdiC7 (/member/MehdiC7/) 2 years ago

Reply


Upvote

i need to control stepper motor without libraries ..

(/member/Matias+IvanM/) Matias IvanM (/member/Matias+IvanM/) 2 years ago

Good tutorial, but could you explain with a simple schema, how to make the correct connection to use a bipolar stepper with this Dual controller?

Thank you for the tutorial

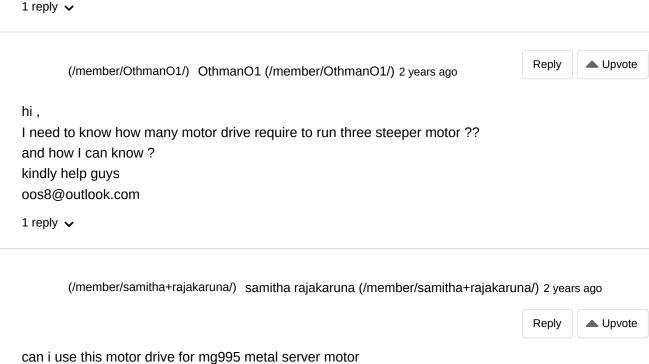

(/member/Tanoshimi2000/) Tanoshimi2000 (/member/Tanoshimi2000/) 2 years ago

Reply Upvote

I want to set this up to have a 12V Drill Motor connected to L298N and Arduino, plugged into a 12V wall power supply for power, and the USB port for sending commands to the motor. Is there a difference in wiring it this way? Also, is it a problem to have the 12V wall power supply, but then also have 5V from the USB that's connected for data?

More Comments

Post Comment

### Categories

Circuits (/circuits/)

**f** Living (/living/) Outside

Workshop (/workshop/) (/outside/) **X** Craft

**Teachers** (/teachers/)

O' Cooking (/cooking/)

(/craft/)

### About Us


Who We Are (/about/) Why Publish? (/create/) Jobs (/community/Positionsavailable-at-

Instructables/)
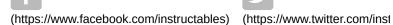
### Resources

Sitemap (/sitemap/) Help (/id/how-towrite-a-greatinstructable/) Contact (/contact/)

(https://www.pinterest.com/instructables)





© 2019 Autodesk, Inc. Terms of Service (http://usa.autodesk.com/adsk/servlet/item?siteID=123112&id=21959721) Privacy Statement (http://usa.autodesk.com/adsk/servlet/item?siteID=123112&id=21292079) Privacy settings

> Legal Notices & Trademarks (http://usa.autodesk.com/legal-notices-trademarks/) (http://www.autodesk.com)